

4-bit Universal shift using VHDL and implement on FPGA:

VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_arith.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity usr is
    Port ( Clk,rst,sin : in  STD_LOGIC;
           m : in  STD_LOGIC_VECTOR (1 downto 0);
           pin : in  STD_LOGIC_VECTOR (3 downto 0);
           sout : out STD_LOGIC;
           pout : out STD_LOGIC_VECTOR (3 downto 0));
end usr;

architecture Behavioral of usr is
    signal p1,p2:std_logic_vector(3 downto 0);
    signal s1:std_logic;
    signal temp:std_logic_vector(22 downto 0);
    signal sclk:std_logic;

    begin
        p11: process(clk,rst)
            begin
                if(rst='1')then temp<=(others=>'0');
                elsif(clk'event and clk='1')
                then
                    temp<= temp + 1;
                end if;
            end process;

            sclk<=temp(22);

        p22:process(sclk,rst,pin,sin,m)
            begin
                if(rst='1') then
                    p1<="0000";
                    p2<="0000";
                    s1<='0';
                elsif (sclk'event and sclk='1') then
                    if(m="00") then    --SISO
                        p1(0)<=sin;
                        p1(1)<=p1(0);
                        p1(2)<=p1(1);
                        p1(3)<=p1(2);
                        s1<=p1(3);
                    elsif (m="01") then    --SIPO
                        p1(0)<=sin;
                        p1(1)<=p1(0);
                        p1(2)<=p1(1);
                        p1(3)<=p1(2);
                        p2<=p1;
                    elsif(m="10") then    --PIPO
                        p1<=pin;
                        p2<=p1;
                    else
                        --PISO
                        p1<=pin;
                        s1<=p1(3);
                    end if;
                end if;
            end process;

            pout<=p2;
            sout<=s1;
        end Behavioral;
```

UCF File:

NET "CLK" LOC = "L15";

onBoardLeds

NET "pout<0>" LOC = "U18";

NET "pout<1>" LOC = "M14";

NET "pout<2>" LOC = "N14";

NET "pout<3>" LOC = "L14";

NET "Sout" LOC = "M13";

onBoard SWITCHES

NET "pin<0>" LOC = "A10";

NET "pin<1>" LOC = "D14";

NET "pin<2>" LOC = "C14";


NET "pin<3>" LOC = "P15";

NET "sin" LOC = "P12";

NET "rst" LOC = "R5";

NET "m<0>" LOC = "T5";

NET "m<1>" LOC = "E4

 

Implementation on FPGA Board:

